
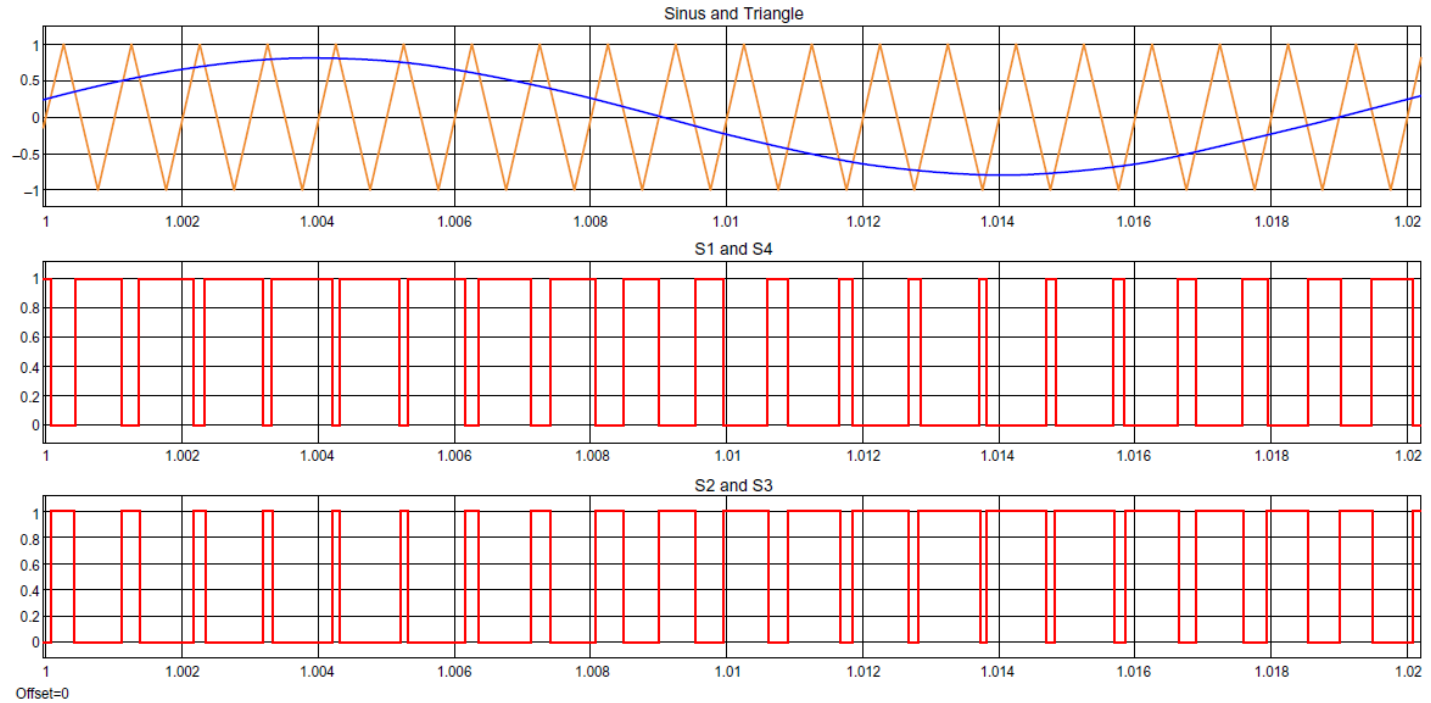


Voltage Control of Single-Phase Inverters



- Commonly-used Techniques
 - Bipolar Sinusoidal-Pulse-Width-Modulation
 - Unipolar Sinusoidal-Pulse-Width-Modulation
 - Single-Pulse-Width-Modulation
 - Multiple-Pulse-Width-Modulation
 - Sinusoidal-Pulse-Width-Modulation
 - Modified-Sinusoidal-Pulse-Width-Modulation
 - Phase-Displacement Control

□ Bipolar SPWM

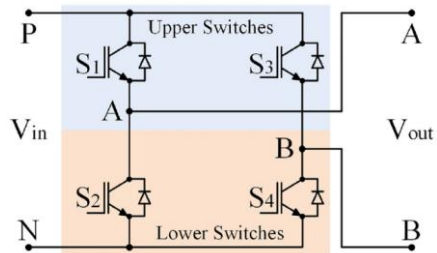



Switching state	“ON” state switches	“OFF” state switches	V_{out}
Positive half-cycle	S_1 - S_4	S_2 - S_3	$+V_{DC}$
Negative half-cycle	S_2 - S_3	S_1 - S_4	$-V_{DC}$

□ Unipolar SPWM

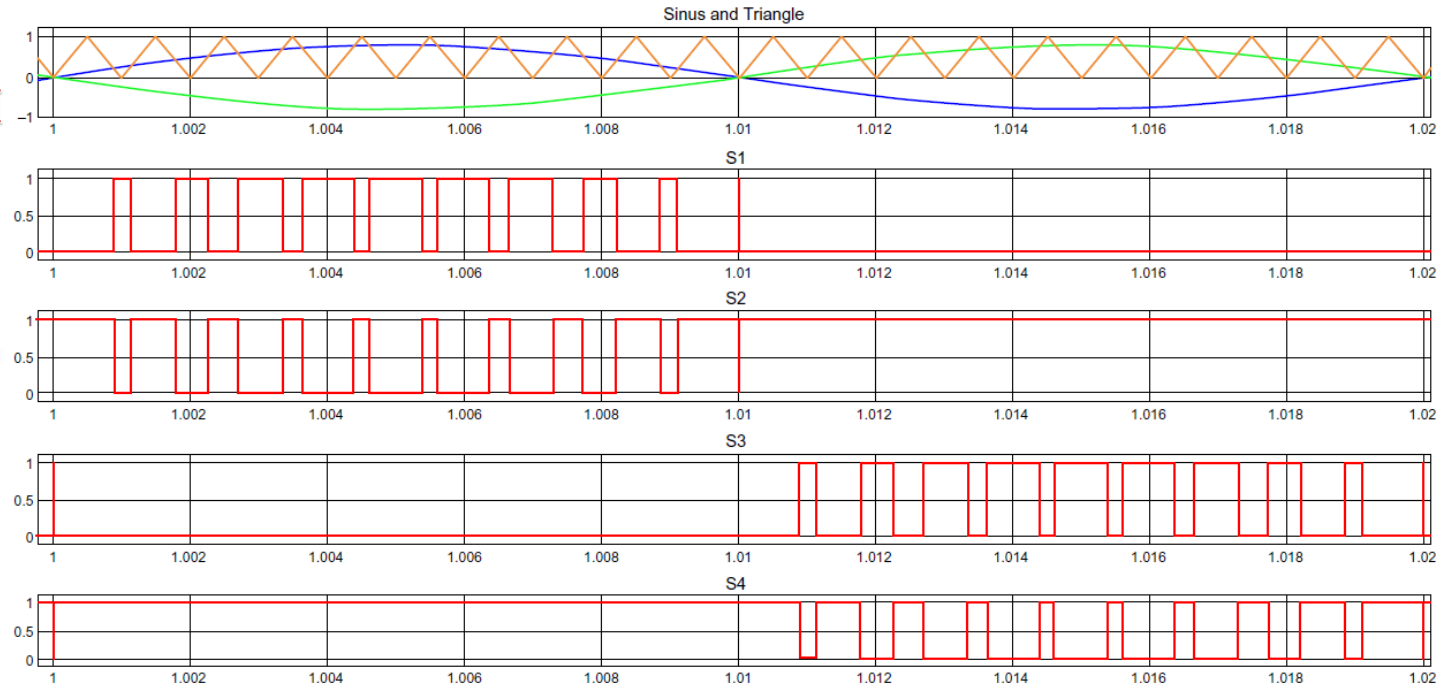
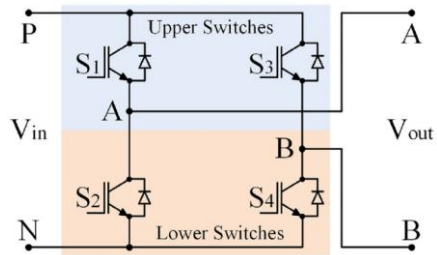


Switching state	“ON” state switches	“OFF” state switches	V_{out}
Positive half-cycle	S_1 - S_4	S_2 - S_3	$+V_{DC}$
Freewheeling mode-I	S_2 - S_4	S_1 - S_3	0
Freewheeling mode-II	S_1 - S_3	S_2 - S_4	0
Negative half-cycle	S_2 - S_3	S_1 - S_4	$-V_{DC}$

Single-Pulse-Width-Modulation

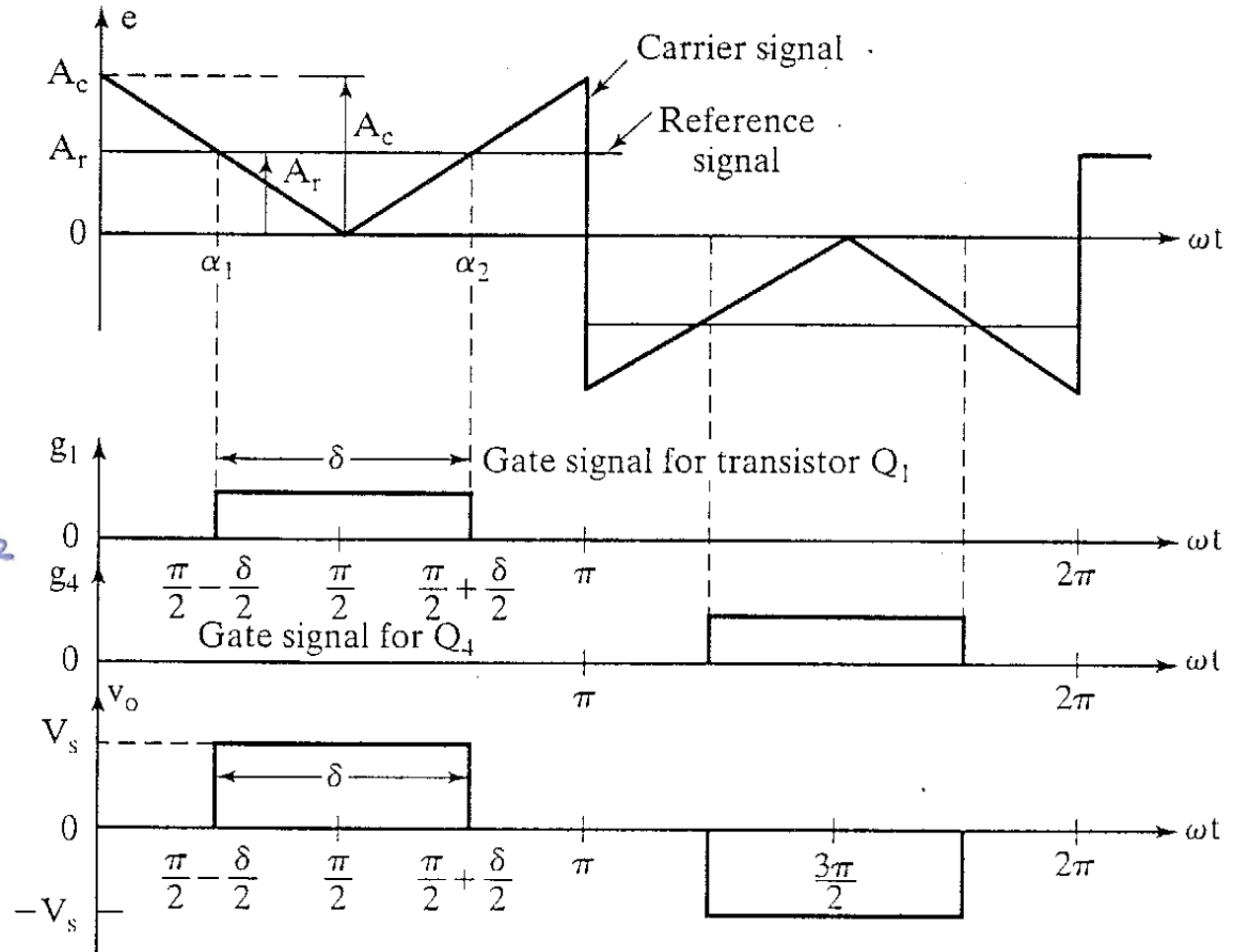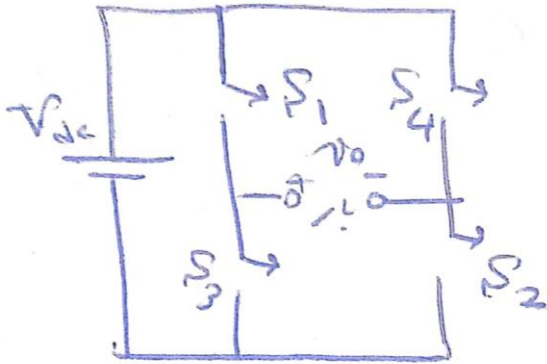


Single-Pulse-Width-Modulation

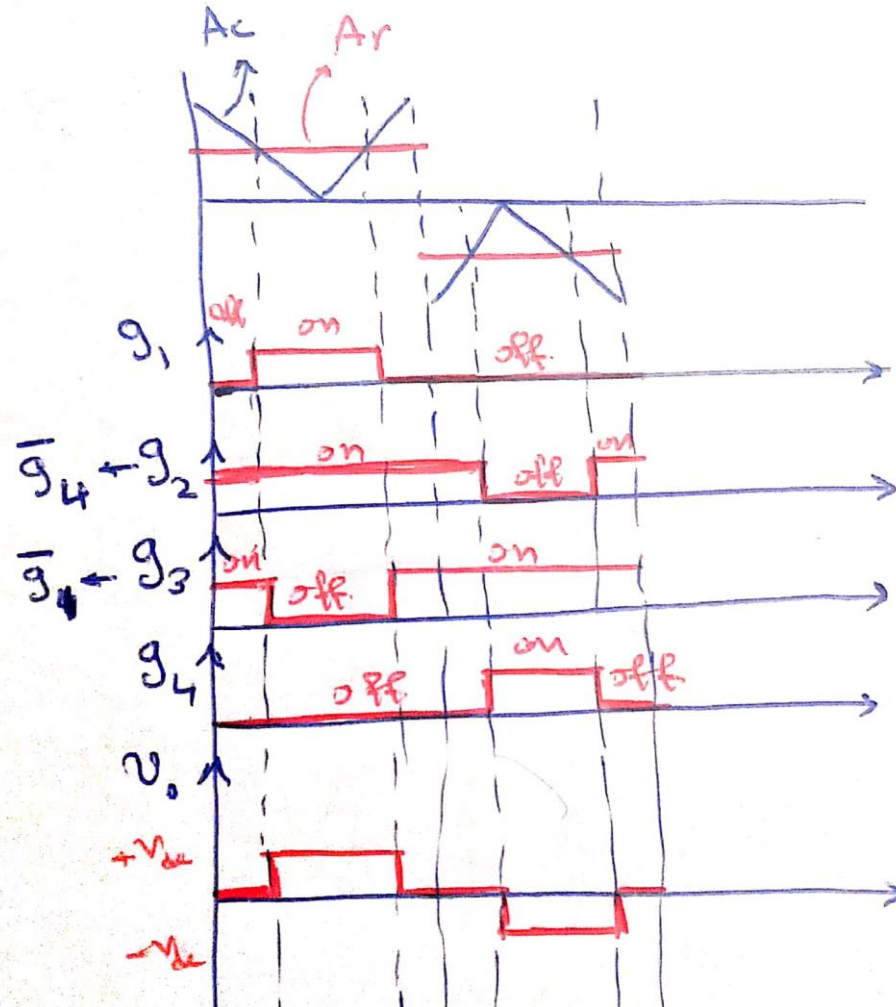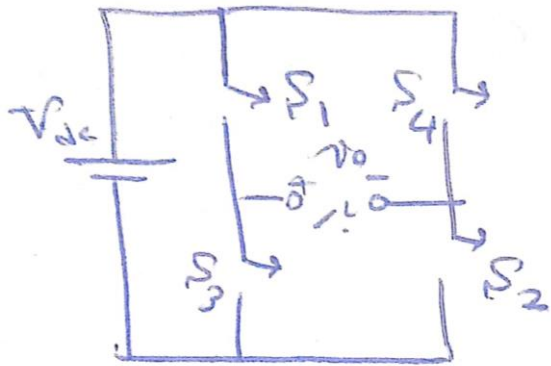


One Pulse per Half-Cycle

Pulse Width Controls the Output Voltage

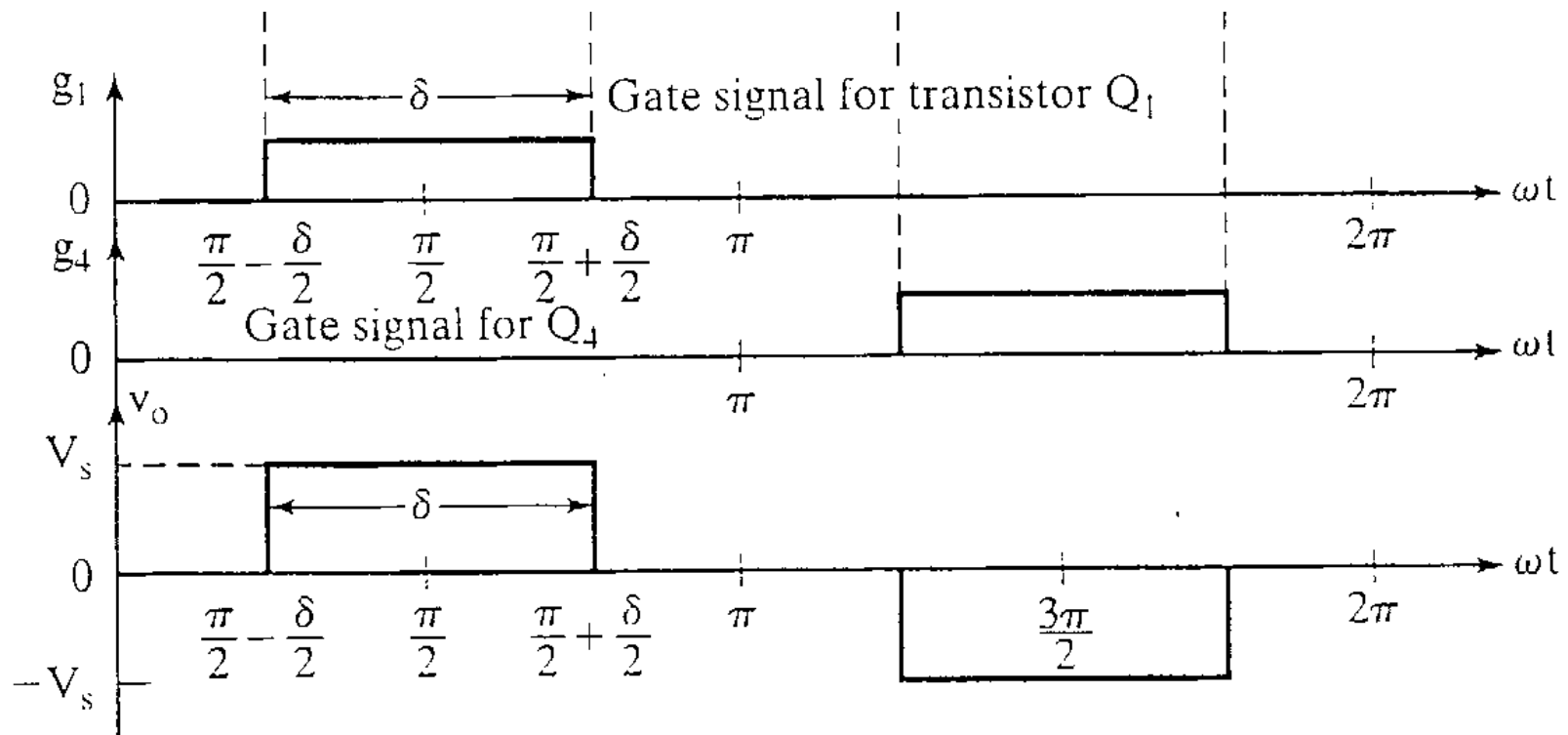

rms value of the Output Voltage

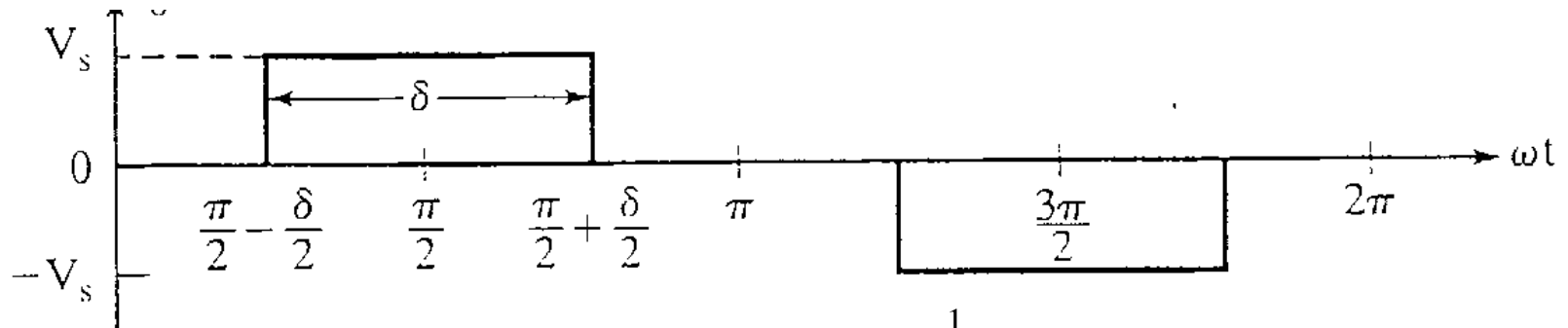


$$V_o = \left[\frac{2}{2\pi} \int_{\frac{\pi-\delta}{2}}^{\frac{\pi+\delta}{2}} V_s^2 d(\omega t) \right]^{\frac{1}{2}}$$

$$V_o = V_s \sqrt{\frac{\delta}{\pi}}$$

$$0^\circ \leq \delta \leq 180^\circ$$


$$0 \leq V_o \leq V_s$$

Fourier Series for the Output Voltage

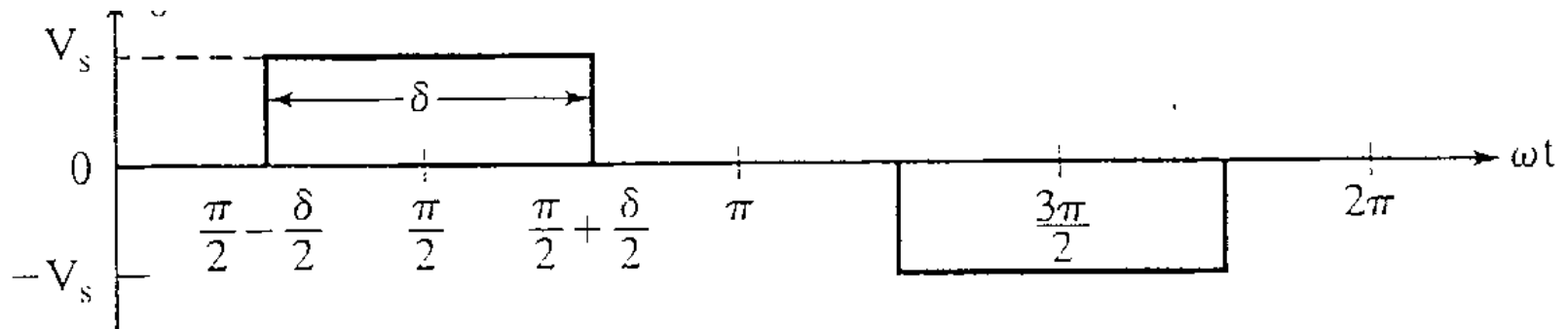


$$v_o(t) = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \sin \frac{n\delta}{2} \sin n\omega t$$


Harmonic Profile

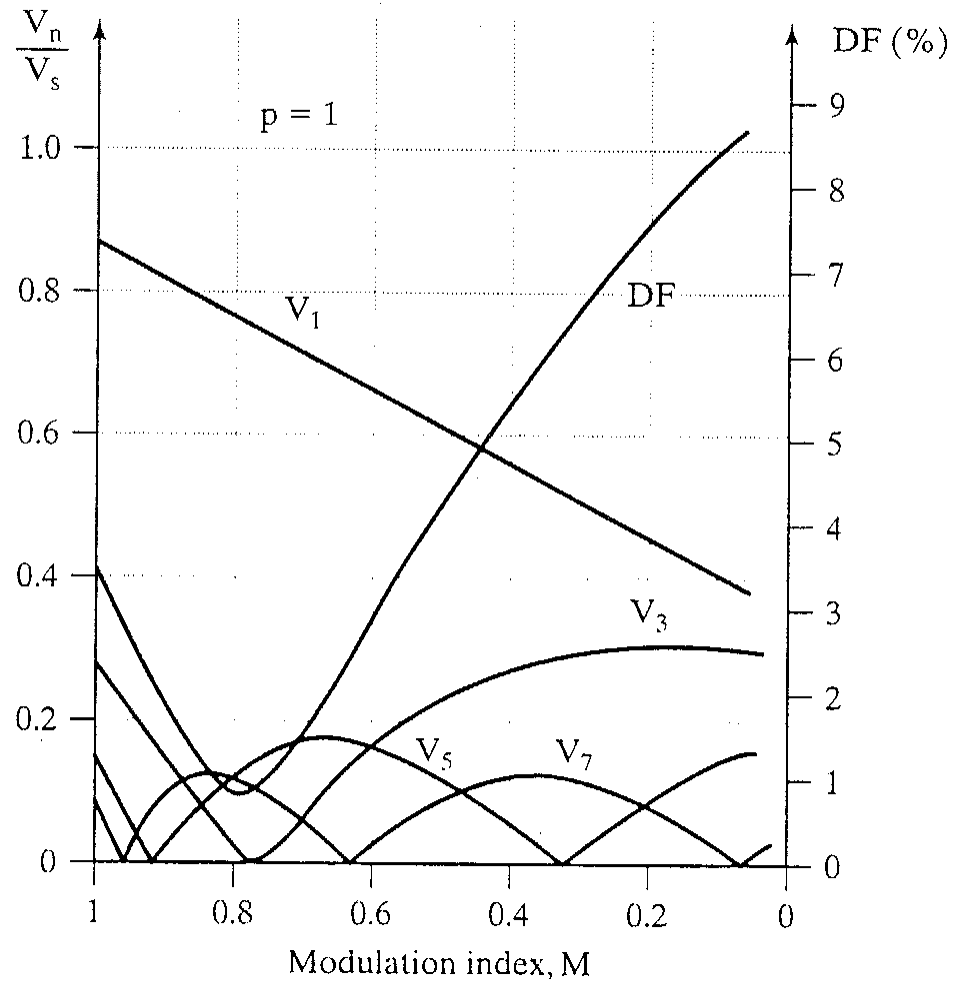


Multiple-Pulse-Width-Modulation

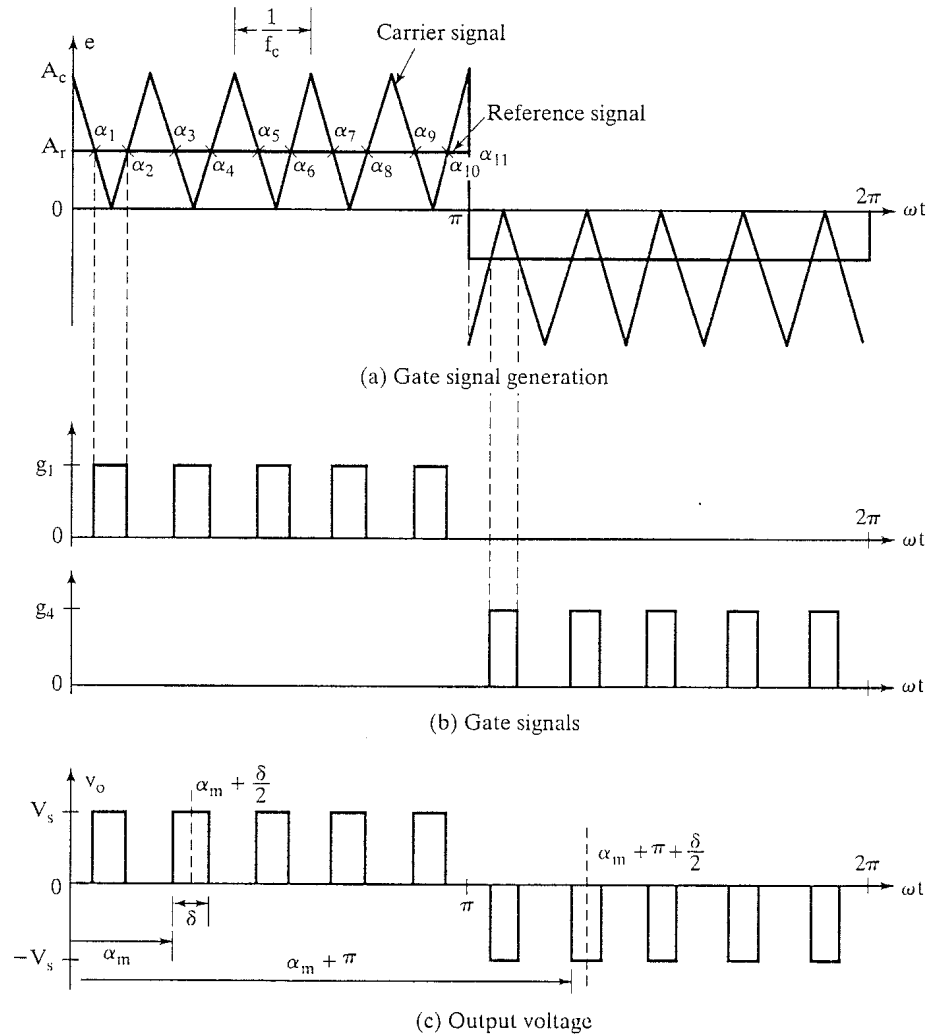

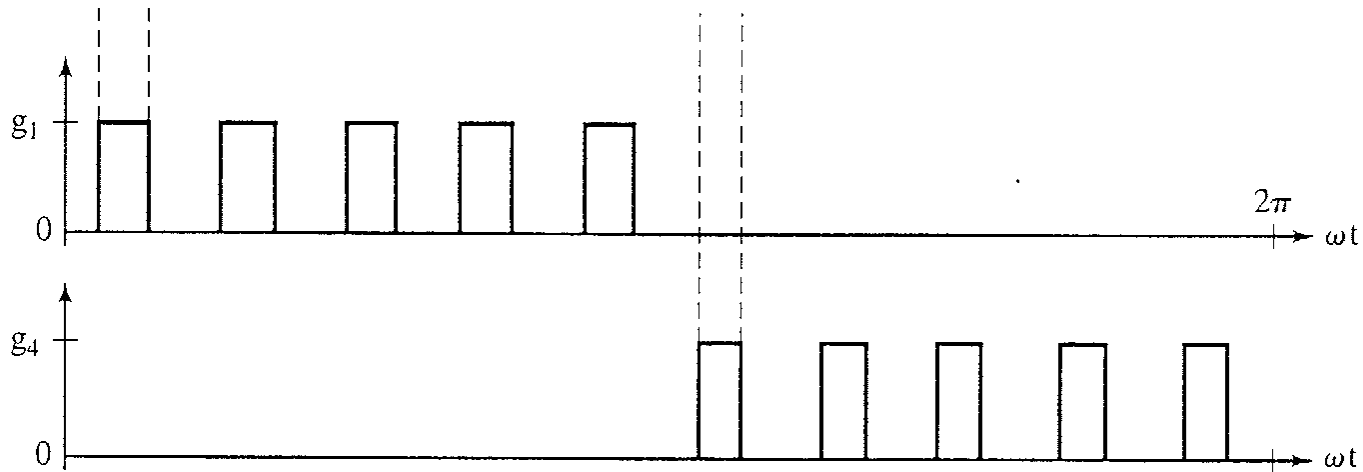Multiple Pulses per Half-Cycle of Output Voltage




(b) Gate signals

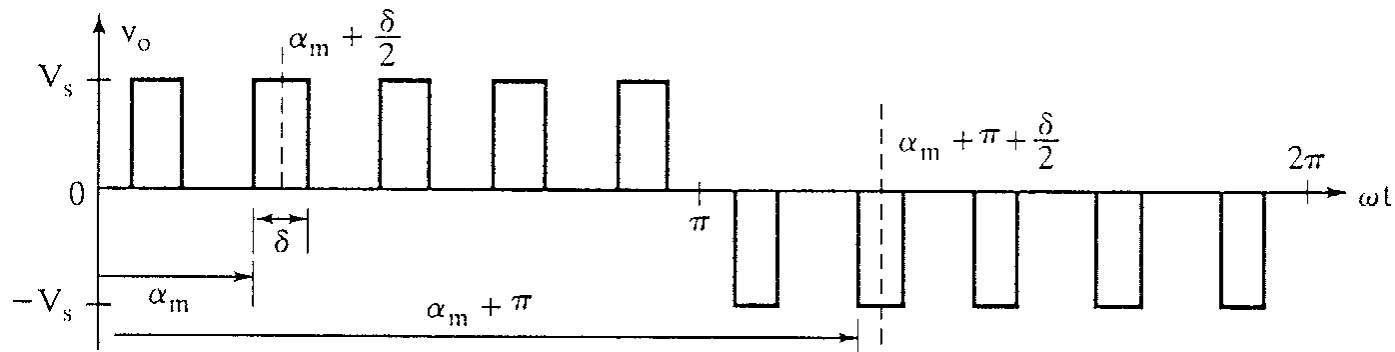


(c) Output voltage

Gate Signal Generation

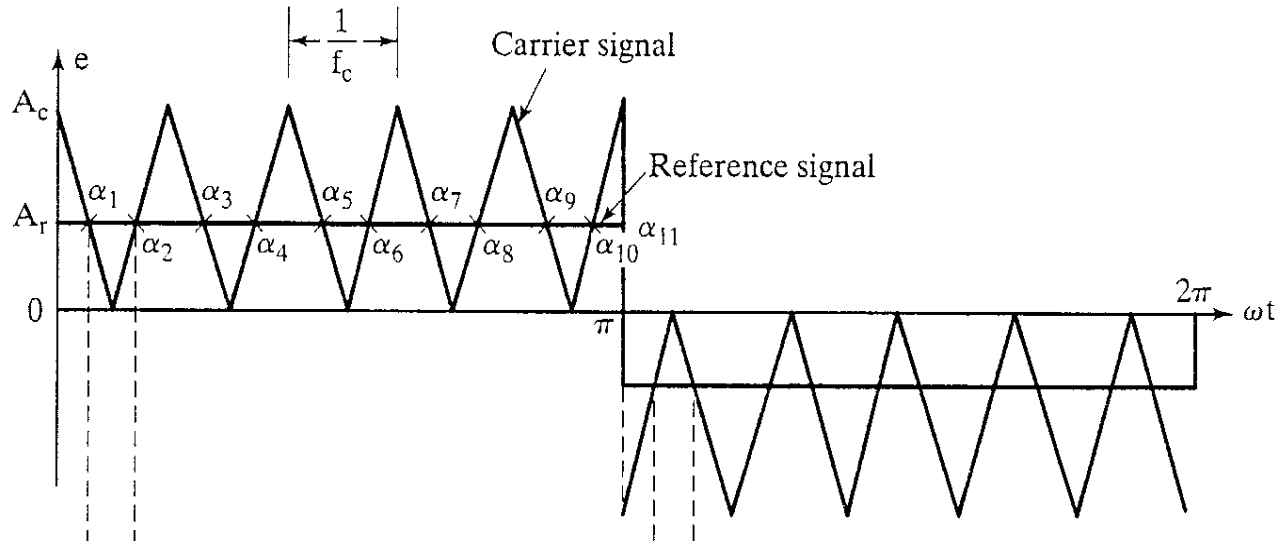


- Compare the Reference Signal with the Carrier
- Frequency of the Reference Signal determines the Output Voltage Frequency
- Frequency of the Carrier determines the number of pulses per half-cycle
- Modulation Index controls the Output Voltage

Gate Signals and Output Voltage

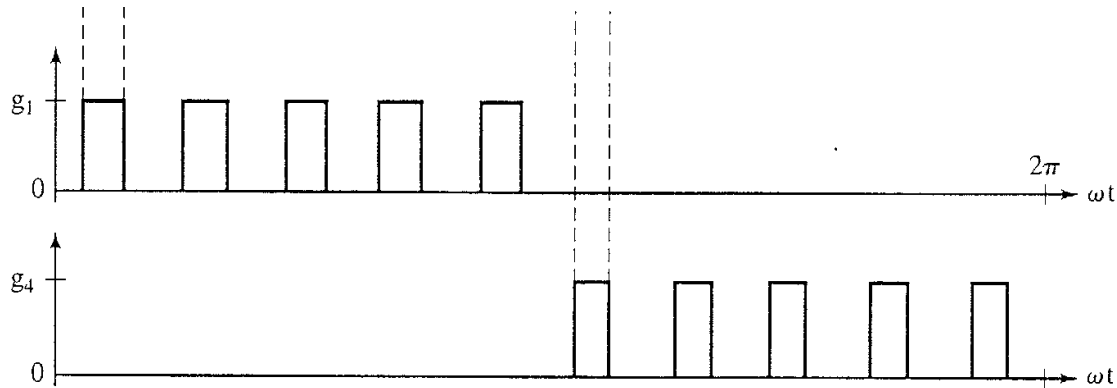

(b) Gate signals

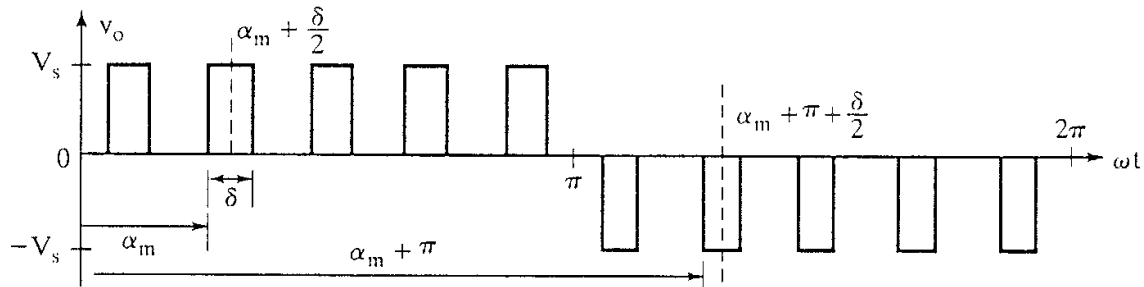

(c) Output voltage

Number of pulses per half cycle = $p = f_c/f_r = m_f$
 where m_f = frequency modulation ratio

rms Value of the Output Voltage

$$V_o = \left[\frac{2p}{2\pi} \int_{(\frac{\pi-\delta}{p})/2}^{(\frac{\pi+\delta}{p})/2} V_s^2 d(\omega t) \right]^{\frac{1}{2}}$$

$$V_o = V_s \sqrt{\frac{p\delta}{\pi}}$$


$$0 \leq M \leq 1$$

$$0 \leq \delta \leq \frac{T}{2p}$$

$$0 \leq \delta \leq \frac{\pi}{p}$$

$$0 \leq V_o \leq V_s$$

Fourier Series of the Output Voltage

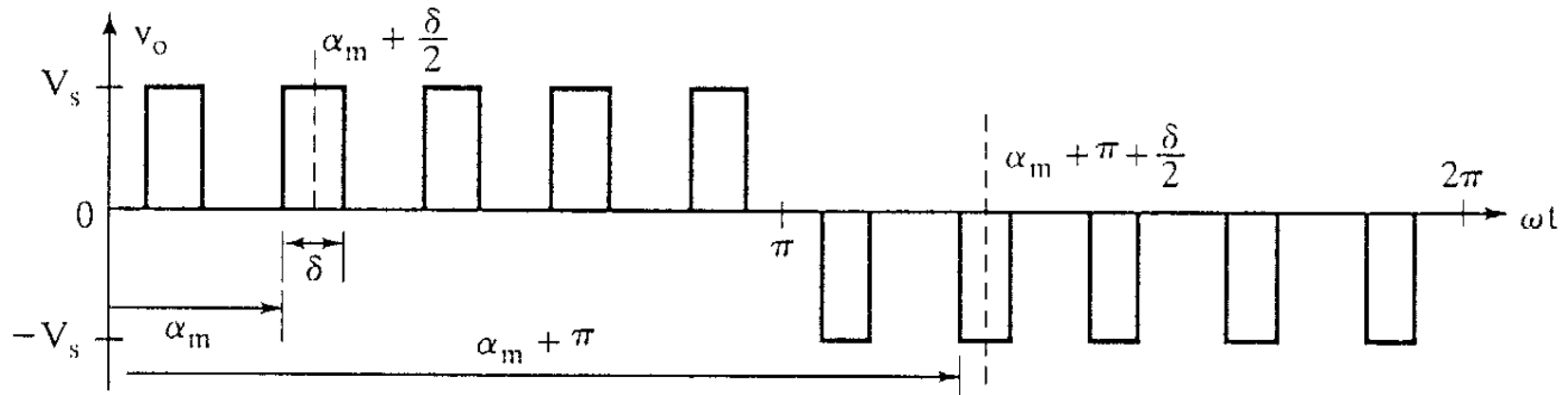

$$v_o(t) = \sum_{n=1,3,5,\dots}^{\infty} B_n \sin n\omega t$$

$$B_n = \sum_{m=1}^{2p} \frac{4V_s}{n\pi} \sin \frac{n\delta}{4} \left[\sin n\left(\alpha_m + \frac{3\delta}{4}\right) - \sin n\left(\pi + \alpha_m + \frac{\delta}{4}\right) \right]$$

Harmonic Profile

